

Register Number :

--	--	--	--	--	--

Subject Code : **40 (NS)****ELECTRONICS**

Time : 3 Hours 15 Minutes]

[Total No. of questions : 37]

[Max. Marks : 70

- Instructions :**
- i) *Question paper has four Parts A, B, C and D.*
 - ii) *Part - A has no choice.*
 - iii) *Part - D has two Parts.*
I – problems.
II – essay type questions.
 - iv) *Draw the circuit diagrams wherever necessary.*
 - v) *Read the instructions given for each part.*

PART – AAnswer **all** questions :**(10 × 1 = 10)**

- 1) Draw the symbol of P-channel JFET.
- 2) What is heat sink?
- 3) Mention the principle used in crystal oscillator.
- 4) Define silent zone in a radio communication.



40 (NS)

- 5) How many side bands are present in AM-wave?
- 6) What is the value of IF for FM – Receiver?
- 7) What is meant by redundant group?
- 8) Convert $(1100)_2$ into Gray code.
- 9) What is the size of an integer in C-programming?
- 10) Expand CDMA.

PART – B

Answer any five questions :

(5 × 2 = 10)

- 11) Mention the different types of transistor biasing.
- 12) Write the steps involved in DC-equivalent circuit of a CE-amplifier.
- 13) What are the advantages of negative feedback amplifier?
- 14) Define CMRR. Give its value for ideal Op-Amp.
- 15) State the Barkhausen criterion for sustained oscillations.
- 16) Mention different types of addressing modes in 8051.



- 17) Write the syntax for 'if-else' statement.
- 18) Mention the important techniques used for Bluetooth operation.

PART - C

Answer **any five** questions :

(5 × 3 = 15)

- 19) Explain the working of N-channel JFET.
- 20) Derive the expression for input impedance for voltage series negative feedback amplifier.
- 21) Draw the circuit diagram and explain Op-Amp as an inverting amplifier.
- 22) Explain the role of Ionosphere in a radio communication.
- 23) Draw the circuit diagram and explain the working of a linear diode detector.
- 24) At what firing angle does SCR of FWR must be triggered to supply $V_{dc} = 60V$ to a load ; Given $V_{rms} = 110V$.
- 25) Explain the operations of power diode under forward biased condition.
- 26) Explain with diagram the working of satellite transponder system.



PART - D

(3 × 5 = 15)

I. Answer any three questions :

27) For the given CE amplifier circuit using germanium transistor.

Calculate



a) V_2

b) I_E

c) r'_e

d) A_v

Given $r'_e = \frac{52mV}{I_E}$, $V_{BE} = 0.32V$

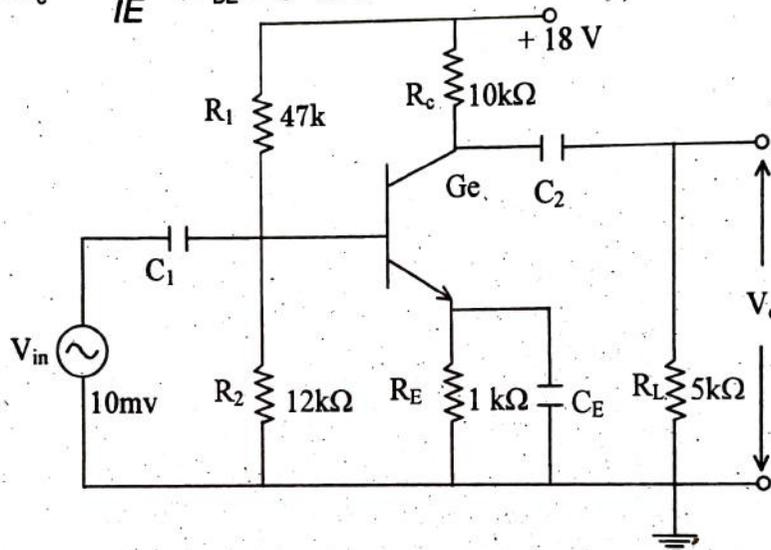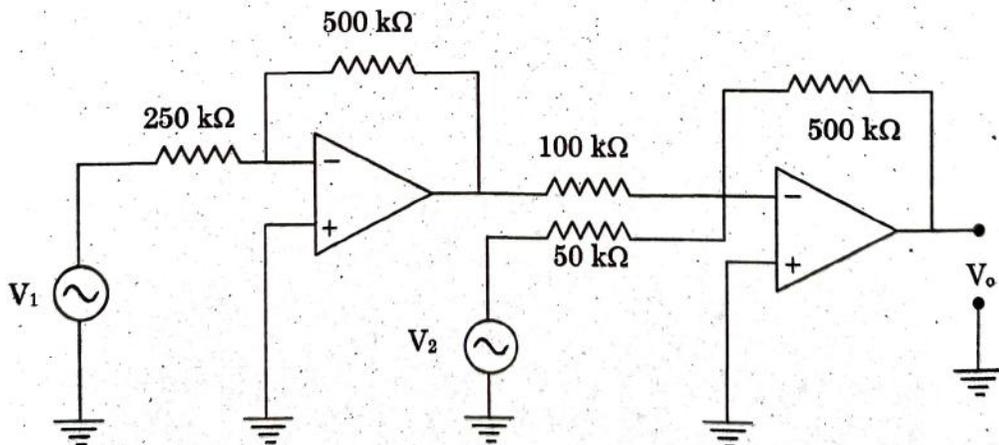28) Calculate the output voltage if $V_1 = 300mv$ and $V_2 = 700mv$ 



29) A transistor colpitts oscillator has $L=10\text{mH}$, $C_1 = 0.1\mu\text{F}$ and $C_2 = 0.1\mu\text{F}$. Determine the frequency of oscillations.

30) A frequency modulated signal is

$$\text{given } V_{\text{FM}} = 10 \sin [6 \times 10^8 t + 5 \sin 1250 t]$$

Determine

- a) carrier frequency
- b) modulating frequency
- c) modulation index
- d) maximum frequency deviation and
- e) power dissipated in a 5Ω resistor.

31) Simplify the Boolean expression. $Y = \sum m(0,1,4,13,15) + \sum d(2,5,7)$ and then draw the logic diagram using only basic gates.

II. Answer any four questions:

(4 × 5 = 20)

32) Explain with circuit diagram, the working of two stage direct coupled CE – amplifier. Draw the frequency response of it.

33) a) What is a differentiator of Op–Amp?

b) Derive an expression for output voltage of an Op–Amp differentiator.
(1+4)

34) a) What is the principle of superhetrodyne AM–receiver.

b) Explain the functions of each block of superhetrodyne AM–receiver.
(2+3)



- 35) What is Full adder? Draw the circuit of Full adder using three input XOR gate and basic gates. Write its truth table.
- 36) Write an assembly language program to multiply 08H and 0BH. What are the contents of register A and register B after the execution of the program.
- 37) (a) What is de-bugging?
- (b) Explain the different types of errors that occur in C-programming language. (1+4)
-